



### MAX4183EUB+

Gawo la Nambala: **MAX4183EUB+**

Mafotokozedwe Akatundu: IC OPAMP CFA 270MHZ 10UMAX

Mkhalidwe wa RoHS: Kutsogolera / RoHS Kumvera

Datasheets: [1.MAX4183EUB+.pdf](#) [2.MAX4183EUB+.pdf](#)

Wopanga / Chinthu: Maxim Integrated

Chombo Chochokera: Hong Kong

Njira Yoperekerana: DHL/Fedex/TNT/UPS/EMS

[TUMIZANI MAFUNSO](#)

Chithunzi chitha kukhala choyimira.  
Onani malongosoledwe azinthu zazamalonda.

### Zambiri zamalonda

<b>Gawo la Nambala</b>	MAX4183EUB+	<b>Wopanga</b>	Maxim Integrated
<b>Kufotokozera</b>	IC OPAMP CFA 270MHZ 10UMAX	<b>Mkhalidwe Wopanda Ufulu / Mkhalidwe wa RoHS</b>	Kutsogolera / RoHS Kumvera
<b>Tsamba lazambiri</b>	1.MAX4183EUB+.pdf 2.MAX4183EUB+.pdf		
<b>Voltage - Supply, Single / Kawiri (±)</b>	270MHz	<b>Mphamvu</b>	1µA
<b>Mpweya - Kutha</b>	10-uMAX	<b>Mndandanda</b>	-
<b>Mkhalidwe wa RoHS</b>	Tube	<b>Kusokoneza</b>	10-TFSOP, 10-MSOP (0.118", 3.00mm Width)
<b>Mtundu Wotsatsa</b>	-	<b>Mafotokozedwe</b>	2
<b>Kutentha Kwambiri</b>	-40°C ~ 85°C	<b>Number of Bits / Stages</b>	1.5mV
<b>Mtundu Wokwera</b>	Surface Mount	<b>Mphuno Yopanda Chisokonezo (MSL)</b>	1 (Unlimited)
<b>Max Output Power x Channels @ Load</b>	Current Feedback	<b>Nambala Yachigawo Chopanga</b>	MAX4183EUB+
<b>Kulongosola kwowonjezereka</b>	Current Feedback Amplifier 2 Circuit 10-uMAX	<b>Kufotokozera</b>	IC OPAMP CFA 270MHZ 10UMAX
<b>Zowonjezera - Supply (Main IC)</b>	4.5 V ~ 11 V, ±2.25 V ~ 5.5 V	<b>Zamakono - Supply</b>	1mA
<b>Zida pa IC</b>	60mA	<b>-3db Bandwidth</b>	450 V/µs

### Zamgululi Related

<p><b>MAX4185EUB+</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 10UMAX Sakanizani: <a href="#">1.MAX4185EUB+.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4184ESA+</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 245MHZ 8SOIC Sakanizani: <a href="#">1.MAX4184ESA+.pdf</a></p> <p><a href="#">RFQ</a></p>
<p><b>MAX4183EUB+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 10UMAX Sakanizani: <a href="#">1.MAX4183EUB+T.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4183EUB</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 10UMAX Sakanizani: <a href="#">1.MAX4183EUB.pdf</a></p> <p><a href="#">RFQ</a></p>
<p><b>MAX4182ESA+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 245MHZ 8SOIC Sakanizani: <a href="#">1.MAX4182ESA+T.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4182ESA+</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 245MHZ 8SOIC Sakanizani: <a href="#">1.MAX4182ESA+.pdf</a></p> <p><a href="#">RFQ</a></p>
<p><b>MAX4181EUT+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ SOT23-6 Sakanizani: <a href="#">1.MAX4181EUT+T.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4184ESA+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 245MHZ 8SOIC Sakanizani: <a href="#">1.MAX4184ESA+T.pdf</a></p> <p><a href="#">RFQ</a></p>
<p><b>MAX4185EUB+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 10UMAX Sakanizani: <a href="#">1.MAX4185EUB+T.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4186ESD+</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 245MHZ 14SOIC Sakanizani: <a href="#">1.MAX4186ESD+.pdf</a></p> <p><a href="#">RFQ</a></p>
<p><b>MAX4183ESD+</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 14SOIC Sakanizani: <a href="#">1.MAX4183ESD+.pdf</a></p> <p><a href="#">RFQ</a></p>	<p><b>MAX4183ESD+T</b> Opanga: Maxim Integrated Kufotokozera: IC OPAMP CFA 270MHZ 14SOIC Sakanizani: <a href="#">1.MAX4183ESD+T.pdf</a></p> <p><a href="#">RFQ</a></p>

### Zogwirizana

Maxim Integrated MAX4183EUB+  
Mtengo wa MAX4183EUB+  
Zolemba pa MAX4183EUB+ PDF  
Msika wa MAX4183EUB+  
Maxim Integrated MAX4183EUB+  
Maxim Integrated MAX4183EUB+

Wopereka MAX4183EUB+  
Zithunzi za MAX4183EUB+  
MAX4183EUB+ Datasheet Yotsitsa  
Gulani MAX4183EUB+  
Wogulitsa Maxim Integrated

Wogulitsa MAX4183EUB+  
Chithunzi cha MAX4183EUB+  
Masamba MAX4183EUB+  
Gulani Maxim Integrated MAX4183EUB+  
Wopereka Maxim Integrated